

ASSIGNMENT

GUNA VARDHAN

gunavardhan.nagamalla@gmail.com

IITH - Future Wireless Communications (FWC)

CONTENTS

1 Question

2 Components


3 State Transition Table

4 Implementation

1 QUESTION

Q.39. The state diagram of a sequence detector is shown below. State S_0 is the initial state of the sequence detector. If the output is 1, then

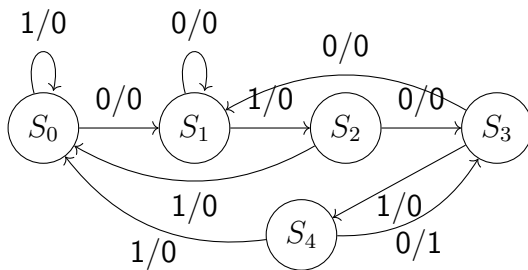- 1) The sequence 01010 is detected
- 2) The sequence 01011 is detected
- 3) The sequence 01110 is detected
- 4) The sequence 01001 is detected



2 COMPONENTS

Component	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	10
Breadboard		1
LED		2
Resistor	220ohms	1

Figure.a

3 STATE TRANSITION TABLE

Truth table Boolean Function "F"

TABLE I: State Transition Table

	Current State	Input (x)	Next State	Output (z)
1	S0	0	S0	0
1	S0	1	S1	0
1	S1	0	S0	0
1	S1	1	S2	0
1	S2	0	S0	0
1	S2	1	S3	1
1	S3	0	S0	0
1	S3	1	S3	1

4 IMPLEMENTATION

Arduino PIN	INPUT	OUTPUT
2	X	
3	Y	
4		Z

Connections

a) Procedure

1. Connect the circuit as per the above table.
2. Connect the output pin to LED
3. Connect inputs to Vcc for logic 1, ground for logic 0
4. Execute the circuit using the below code.

<https://github.com/GUNA5801/FWC/blob/main/AVR-GCC/CODE/main.c>

5. Change the values of X,Y,Z in the code and verify the Truth Table